

¿Cómo medir consumo?

- Potencia
 - Alimentación en DC (fija)
 - Alcanza con medir corriente
 - Medir promedios
 - Medidas instantáneas
- Energía = Potencia * tiempo
- El DUT tiene que estar funcionando!!!!
 - Alimentado
 - Con entradas reales
 - Si tiene software tiene que estar corriendo



Co-funded by the
Erasmus+ Programme
of the European Union

Alternativas


- Amperímetro en serie con la fuente
- Shunt + voltímetro
- VFC: Voltage-to-Frequency Converter
- Espejo de corriente
- Carga/descarga de condensadores
- Celdas de efecto Hall

Amperímetro

- Conectar un amperímetro en serie con la fuente de alimentación
- Problemas:
 - Resistencia interna del amperímetro
 - Mide promedios de I_{cc}
 - Entradas al circuito (input patterns)
 - ¿Periódicas?
 - Ventana de tiempo en la que promedia el amperímetro >> cambios en las entradas



Shunt + Medida de voltaje

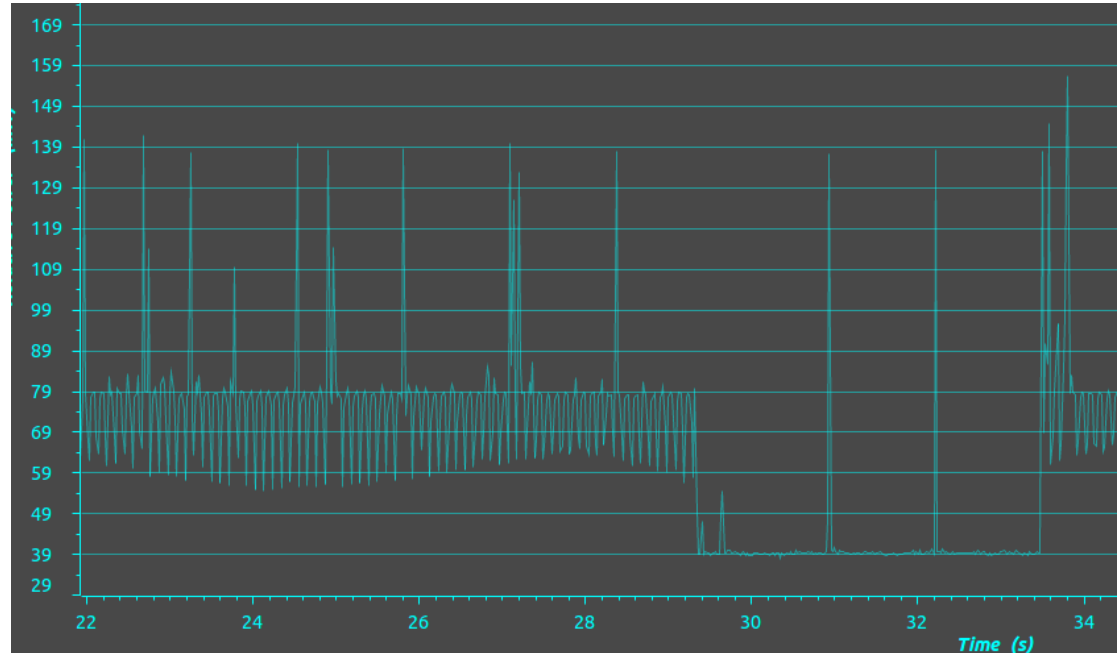- Shunt
 - En VCC o en GND
- Shunt + voltímetro
 - Medida flotante
 - Atención: modo común
- Voltímetro
 - Directo: tester, osciloscopio, A/D
 - Amplificador + voltímetro
- Rango a medir
 - Cambiar shunt?
 - Caídas de voltaje
- Picos de corriente
 - Filtrar con capacitor
 - Integrar numéricamente



Shunt + amp diferencial

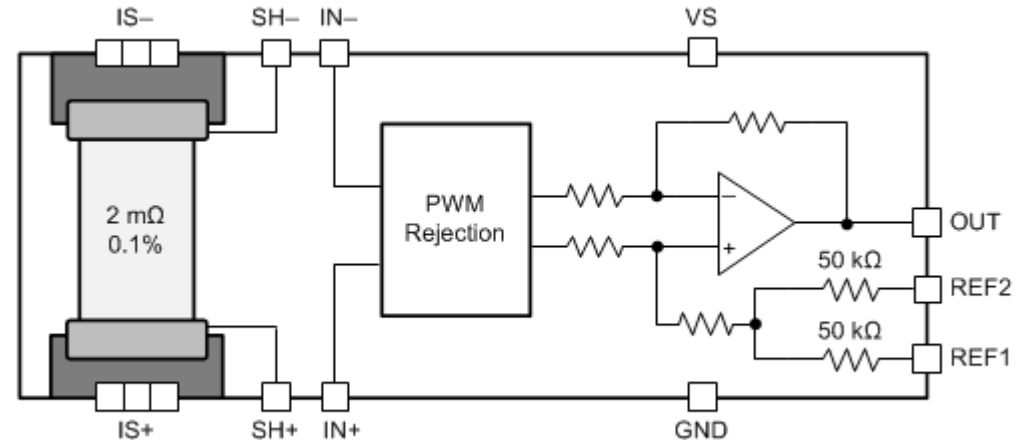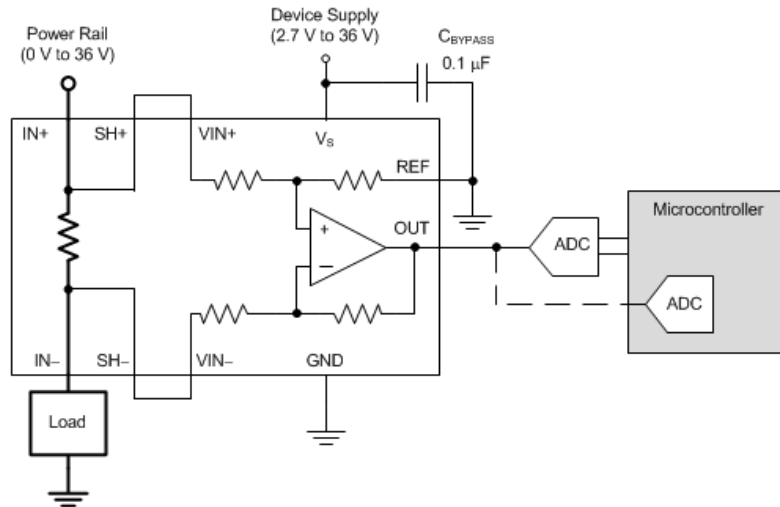- Current sense amplifier with integrated shunt
 - Texas Instrument INA250, INA253



Current Sense Circuit Collection

Current Sense Circuit Collection, Making Sense of Current, Tim Regan, Jon Munson, Greg Zimmer, Michael Stokowski, Application Note 105, December 2005. Linear Technology

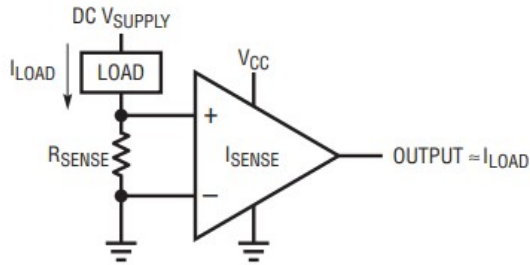


Figure 1. Low Side Current Sensing

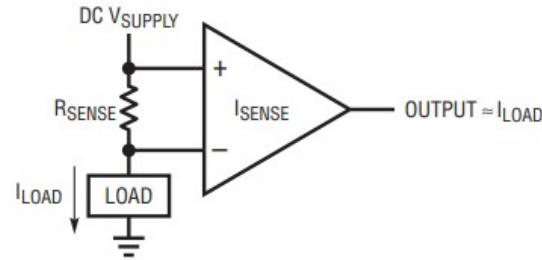


Figure 2. High Side Current Sensing

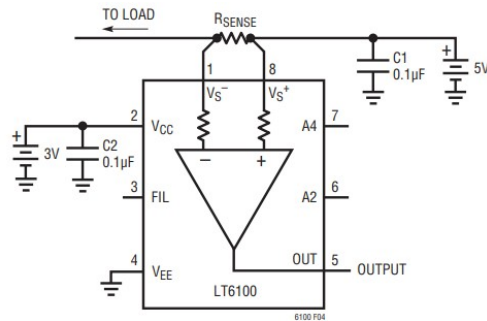


Figure 4. LT6100 Load Current Monitor

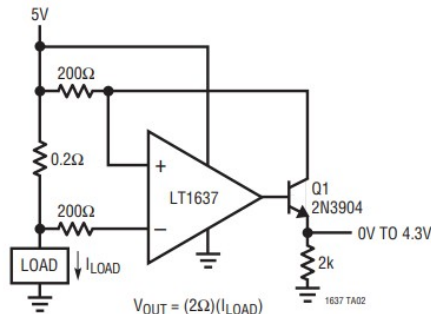


Figure 5. "Classic" Positive Supply Rail Current Sense


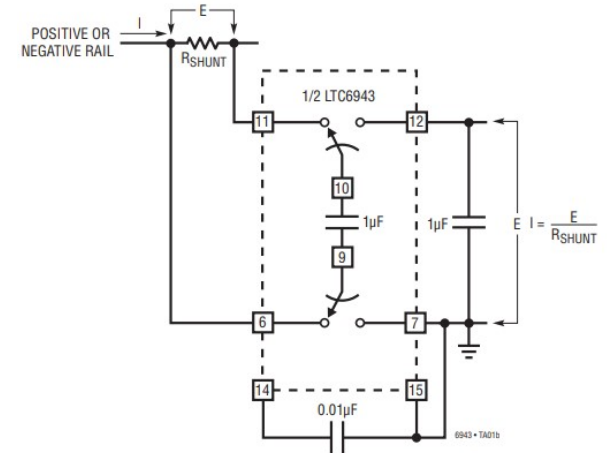


Figure 11. Precision Current Sensing in Supply Rails


EEG compression

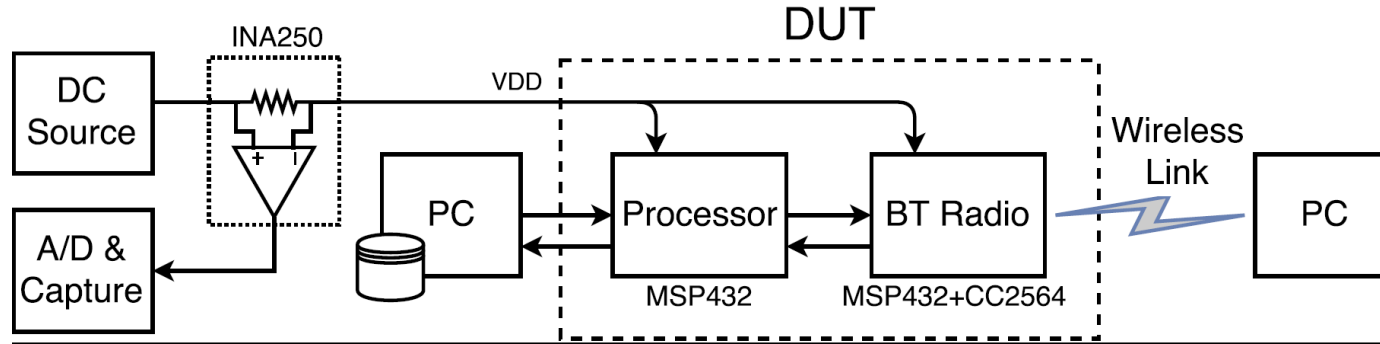

Guillermo Dufort Y Alvarez, Federico Favaro, Federico Lecumberry, Alvaro Martin, Juan P Oliver, Julian Oreggioni, Ignacio Ramirez, Gadiel Seroussi, Leonardo Steinfeld, "Wireless EEG System Achieving High Throughput and Reduced Energy Consumption Through Lossless and Near-Lossless Compression," in IEEE Transactions on Biomedical Circuits and Systems, vol. 12, no. 1, pp. 231-241, Feb. 2018, doi: 10.1109/TBCAS.2017.2779324.


Cycle energy measurements

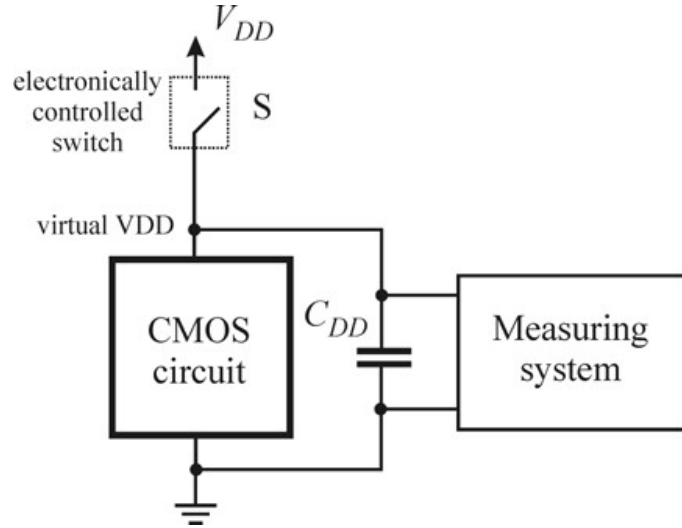Capacitor-based measurement (switched capacitor)




$$E = \frac{1}{2} C_{DD} V_{DD}^2 - \frac{1}{2} C_{DD} (V_{DD} - \Delta V)^2 = E_0 \left[2 \frac{\Delta V}{V_{DD}} - \left(\frac{\Delta V}{V_{DD}} \right)^2 \right]$$

$$E_0 = C_{DD} V_{DD}^2 / 2$$

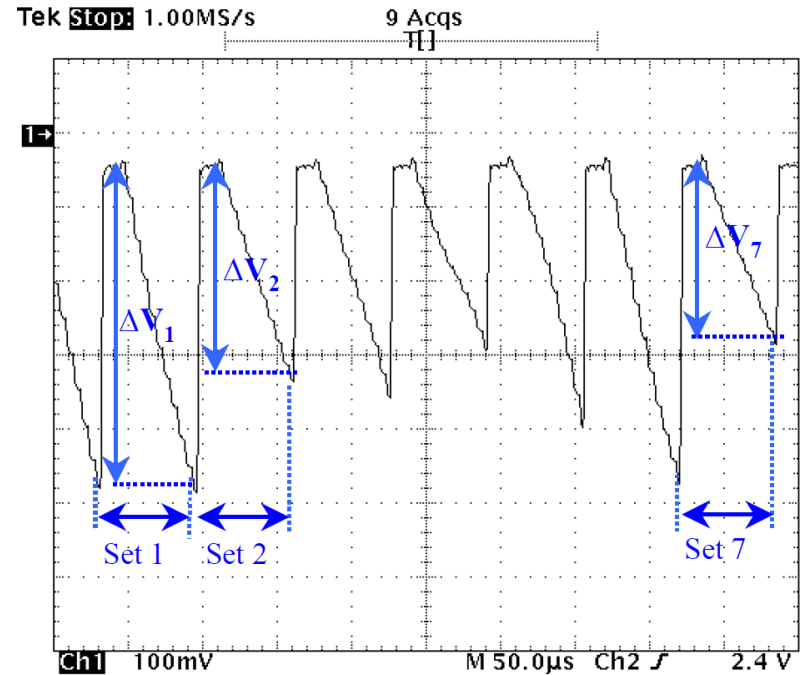

J. Rius-Vazquez, E. Boemo, A. Peidro-Palanca, S. Manich-Bou and R. Rodriguez-Montañes, "Measuring Power and Energy of CMOS Circuits: A Comparative Analysis", Proceedings DCIS 2003 (XVIII Conference on Design of Circuits and Integrated Systems), pp. 89-94, Ciudad Real, November 2003. ISBN: 84-87087-40-X

Método con 2 capacitores

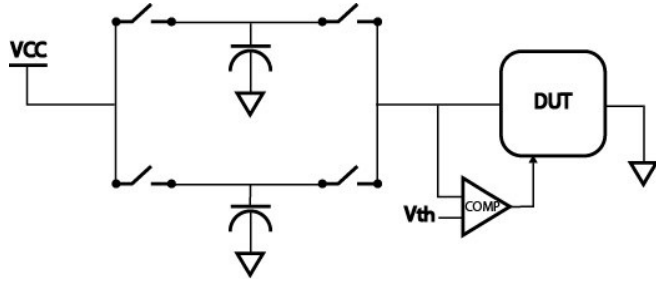


- La diferencia de tensión en los capacitores se utiliza para calcular el consumo del circuito durante un ciclo de trabajo.
- Tensión en C
 - V_0 en el instante t_0
 - V_1 en el instante t_1
- La carga consumida durante el intervalo $t_1 - t_0$ es: $Q_1 - Q_0 = C(V_1 - V_0)$
- Cuando se llega a V_{th} se intercambian los capacitores

Más bibliografía

- J. Oreggioni and L. Steinfeld, "Automedida de consumo en dispositivos portables," in Proceedings of the XIX Iberchip Workshop, Cusco, Peru, 2013. [Online]. Available: <http://iie.fing.edu.uy/publicaciones/2013/OS13>
- Villaverde, J., Bouvier, D. A., Fernández, C., Steinfeld, L., & Oreggioni, J. (2013). Low-Power Self-Energy meter for wireless sensors network. IEEE DCoSS, 315-317
- CHANG, Naehyuck; KIM, Kwanho. Real-time per-cycle energy consumption measurement of digital systems. Electronics Letters, 2000, 36.13: 1169-1171.
- Chang, N., Kim, K. and Lee, H.G., 2000, August. Cycle-accurate energy consumption measurement and analysis: Case study of ARM7TDMI. In Proceedings of the 2000 international symposium on Low power electronics and design (pp. 185-190).
- J. Rius-Vazquez, E. Boemo, A. Peidro-Palanca, S. Manich-Bou and R. Rodriguez-Montañes, "Measuring Power and Energy of CMOS Clrcuits: A Comparative Analysis", Proceedings DCIS 2003 (XVIII Conference on Design of Circuits and Integrated Systems), pp. 89-94, Ciudad Real, November 2003. ISBN: 84-87087-40-X
- Lee, H.G., Lee, K., Choi, Y. and Chang, N., 2005. Cycle-accurate energy measurement and characterization of FPGAs. Analog Integrated Circuits and Signal Processing, 42(3), pp.239-251.
- J. Oliver, F. Veirano, D. Bouvier, and E. Boemo, "A low cost system for self measurements of power consumption in field programmable gate arrays," Journal of Low Power Electronics, vol. 13, no. 1, 2017.

VFC: Voltage-to-Frequency Converter



FPGA automedidor

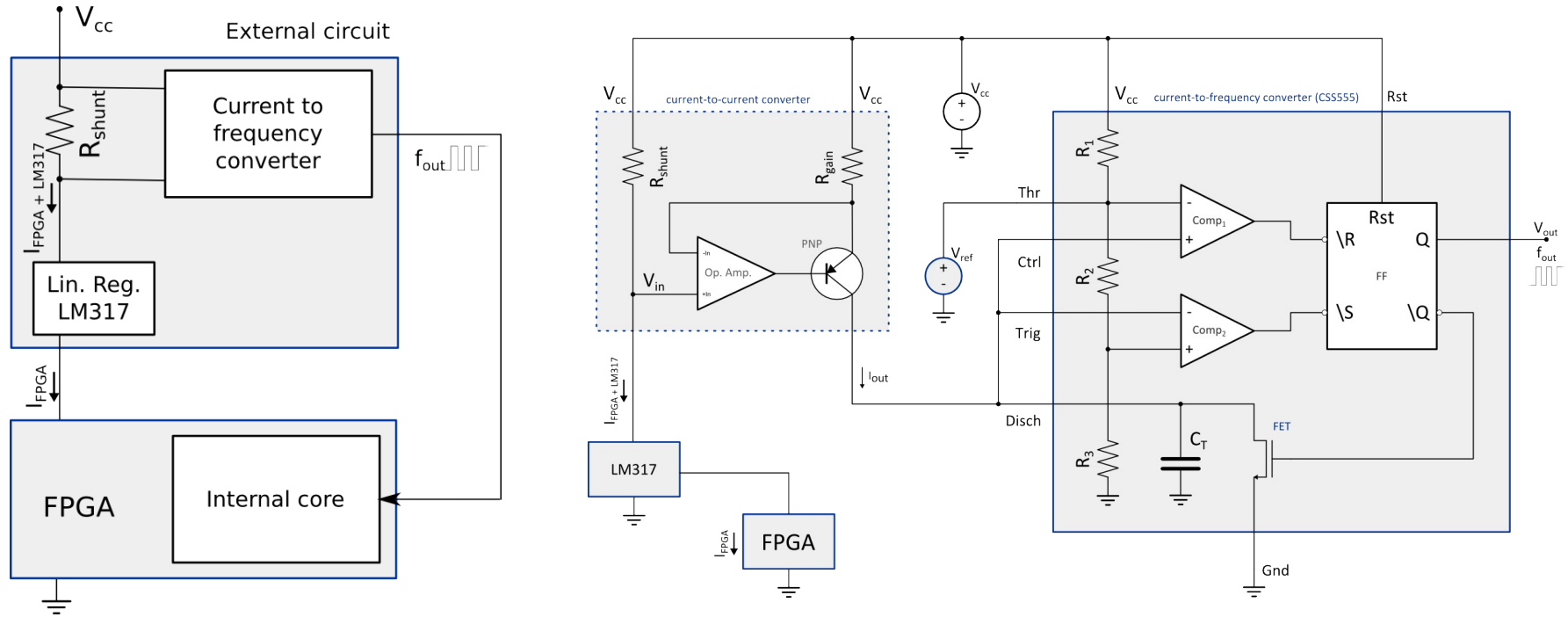

J. Oliver, F. Veirano, D. Bouvier, and E. Boemo, "A low cost system for self measurements of power consumption in field programmable gate arrays," *Journal of Low Power Electronics*, vol. 13, no. 1, 2017.


Hall effect sensor

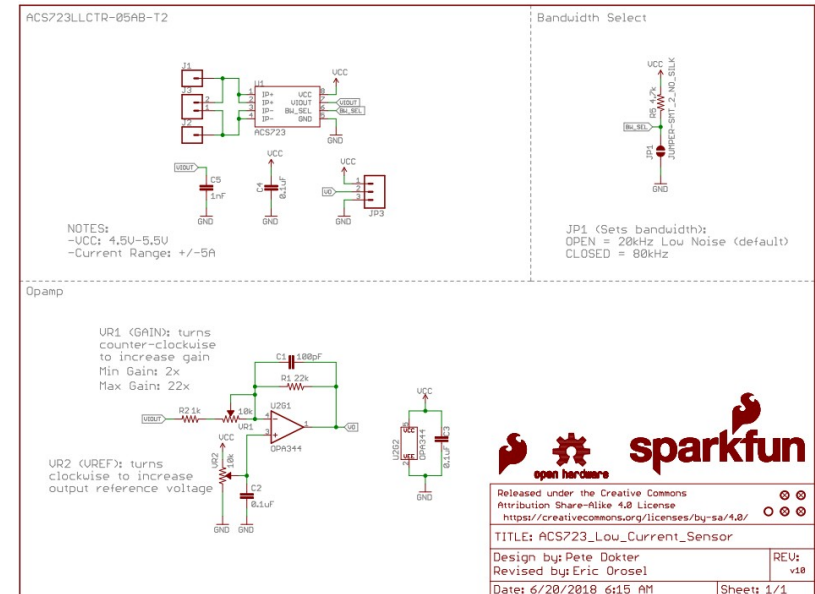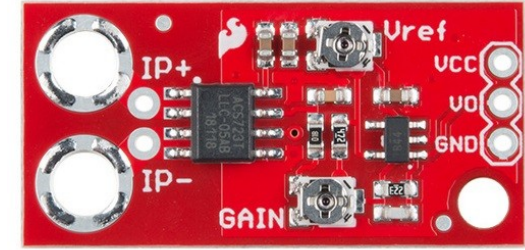- ACS723 Allegro
- High Accuracy, Galvanically Isolated Current Sensor IC
 - +/- 5A, 10A, 20A, 40A
- Sparkfun module: Measures DC and AC currents from around 10mA up to 5A



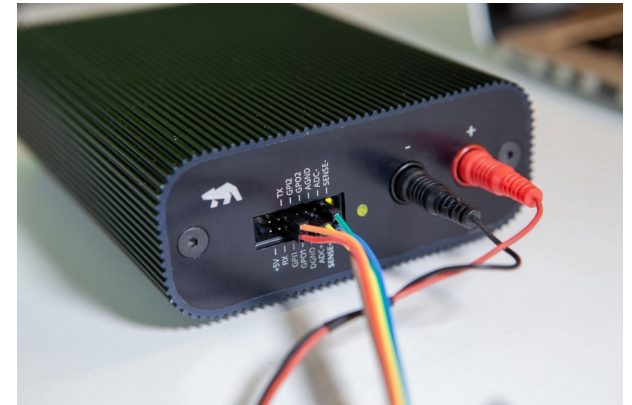Ejemplos de equipamiento específico

- N6705B DC Power Analyzer (Keysight ex Agilent)
- Otii Arc power analyzer and power supply (Qoitech)



N6705B DC Power Analyzer

- 4 power supply, modular
- Voltmeter accuracy: Up to 0.025% + 50 μ V, up to 18 bits
- Ammeter accuracy: Up to 0.025% + 8 nA, up to 18 bits
- Arbitrary waveform generator function: Bandwidth up to 100 kHz, output power up to 300 W
- Scope function: Digitizes voltage and current at up to 200 kHz, up to 18 bits
- Data logger function: Measurement interval from 20 μ s to 60 s
- USD 8500 + DC power modules (600-1000)




<https://www.newark.com/keysight-technologies/n6705c/dc-power-analyzer-current-pow/dp/02A>

C5191
H:\dl\low_power\power_measurements\N6705C - Keysight Technologies - Power Analyzer, Current, Power.mhtml

Otii Arc

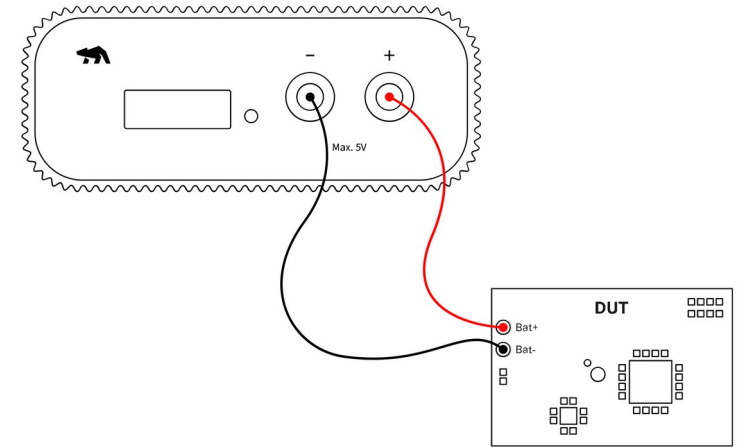- 1 power supply (0.5 V - 3.75 V, 0.5 V - 5.0 V)
- Voltmeter accuracy $\pm(0.1\% + 1.5 \text{ mV})$
 - Sample Rate 1 ksps
- Ammeter accuracy $\pm(0.1\% + 50 \text{ nA})$
 - Sample Rate in $\pm 19 \text{ mA}$ range 4 ksps
 - Sample Rate in $\pm 2.7 \text{ A}$ range 1 ksps
 - Sample Rate in $\pm 5.0 \text{ A}$ range 1 ksps
 - Analog bandwidth (3 dB) 400 Hz
- Extras: UART, A/D, GPIO
- USD 700 + SW



<https://www.qoitech.com/docs/quick-start/connect-otii-arc>


Medidas en placas con FPGAs


- Placa DE0 (Terasic, usada en Dislog y Micro)
 - Sacar regulador, poner uno externo + shunt
- Cómo medir en una DE0-CV
 - Sacar jumper, poner shunt externo
- Cómo medir en una Arty
 - Tiene un shunt + INA199 y un ADC interno en la FPGA
- Cómo medir en la Spartan-6
 - Tiene un shunt + chip PsoC de Cypress (amplificador y ADC)

Placa DE0

Adaptación para medir corriente:

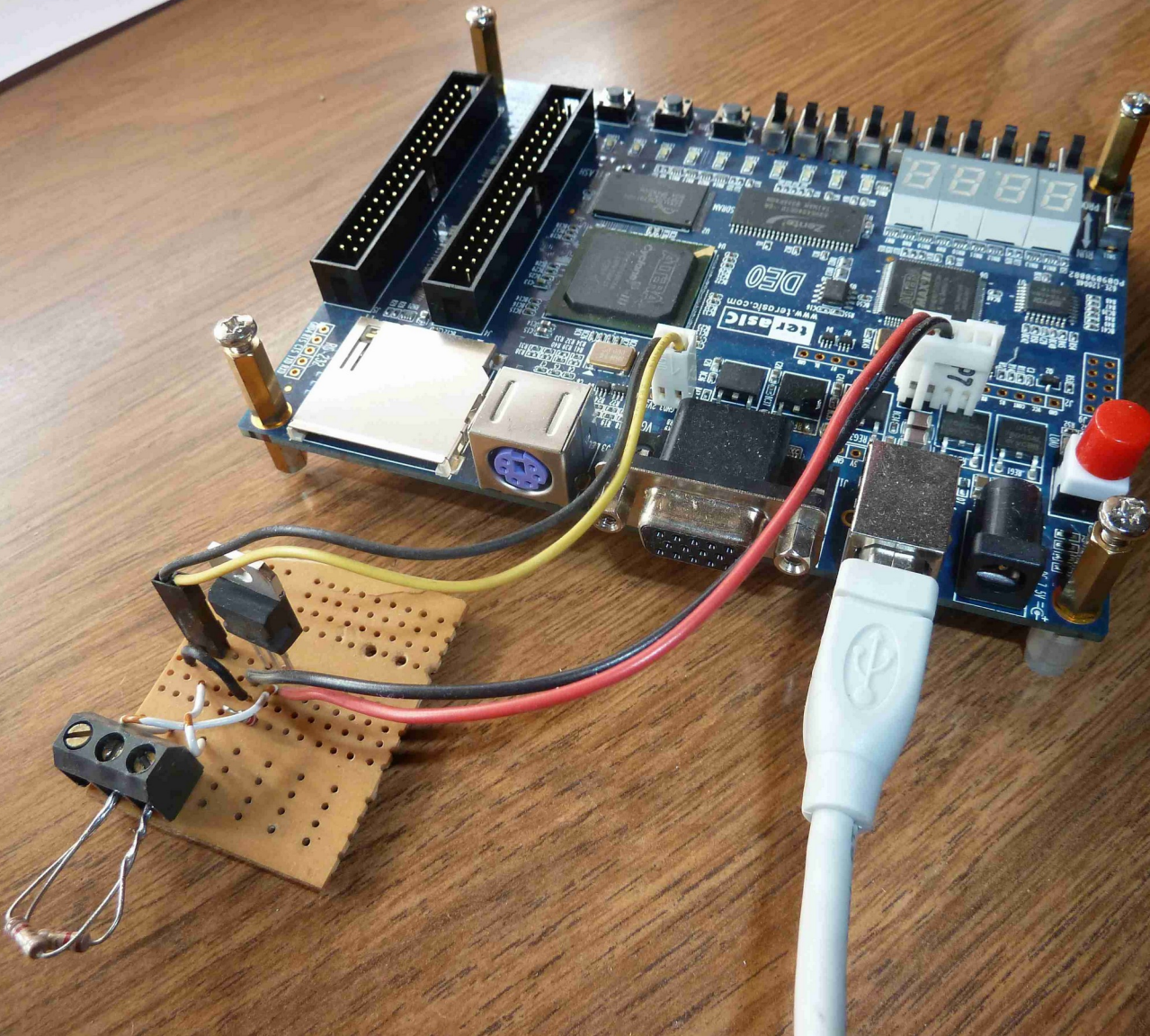- Desoldar regulador original
- Soldar pines de fuentes antes y después del regulador
- Armar placa con regulador externo y shunt



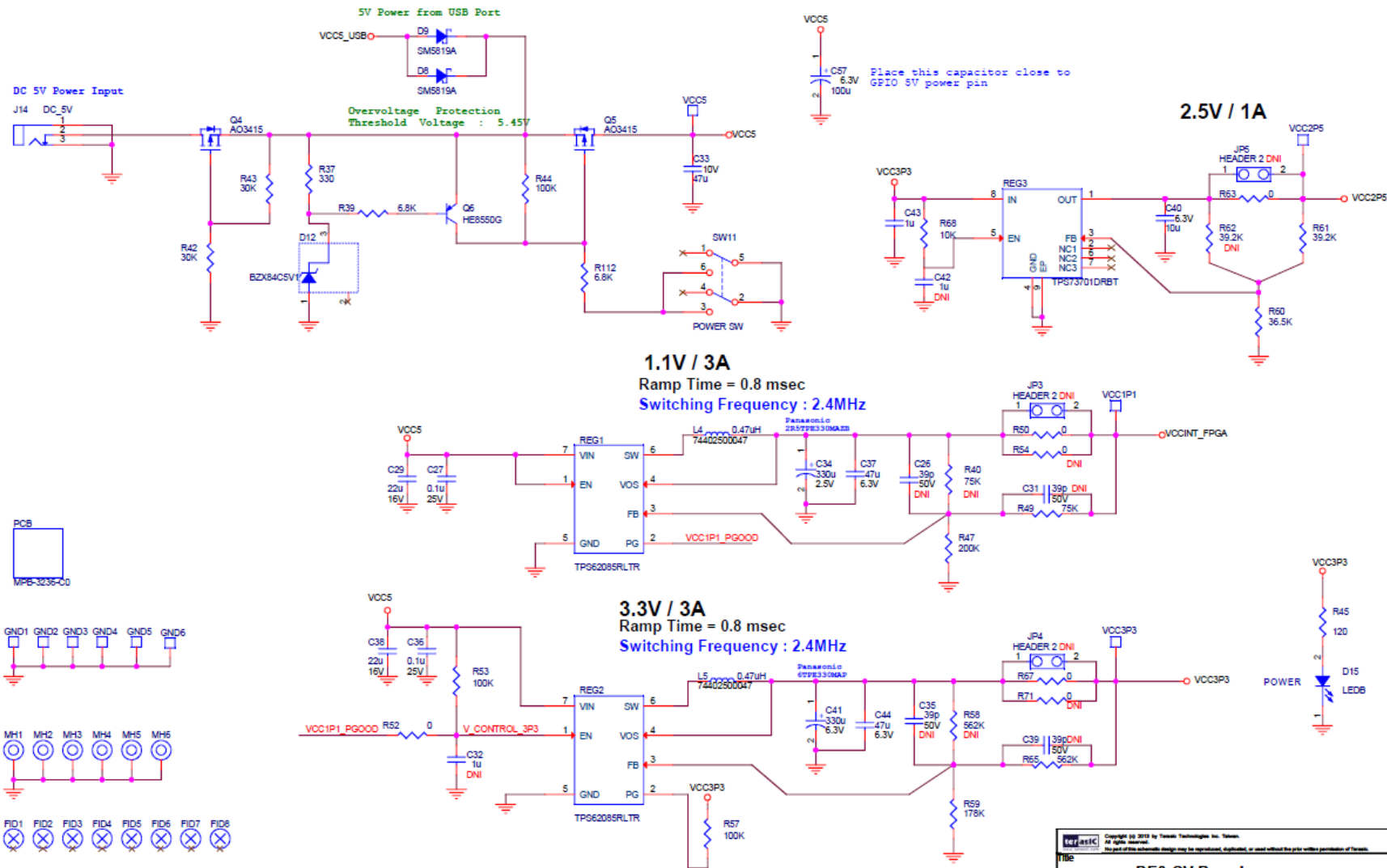

Arty - Digilent

- Ver esquemático Arty
 - INA199A1DCKR Texas
- Artix-7
 - XADC Dual 12-Bit 1 MSPS Analog-to-Digital Converter
- Lectura por USB

Medidas en placas

- Placas que vienen con capacidad de medida
- Analizar esquemático
 - Diferentes fuentes
 - Shunts
 - Reguladores

Sistema funcionando


- Generación de entradas
 - ¿Cuáles?
- Modos de funcionamiento
 - Diferentes módulos encendidos
 - Estados:
 - Bajo consumo
 - Alto consumo

Sistemas Embebidos

- Microcontrolador
 - Varios modos de consumo
- Radio
 - Apagada
 - Encendida, high power, low power
- Medir cada estado y después analizar por software

FPGAs

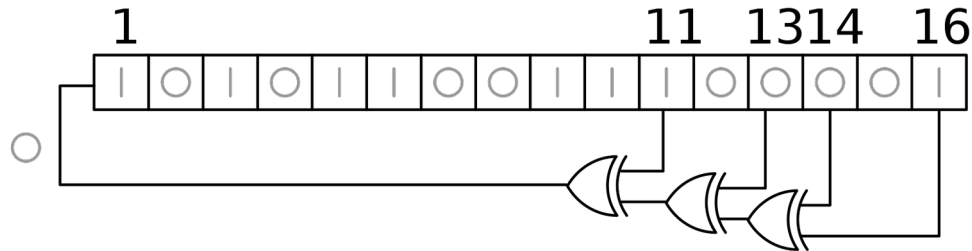- Generador de entradas
 - Reales
 - Pseudoaleatorias
 - Linear Feedback Shift Register LFSR
 - Hay casos que no se pueden usar señales aleatorias



LFSR Pseudo-Random sequence generator

- Any long LFSR counter generates a long pseudo-random sequence of zeros and ones. The sequence is not exactly random since it repeats eventually, and it also follows a mathematically predictable sequence. But for most practical purposes it can be considered random.
- A 63-bit LFSR counter has a repetition time of $(2^{63}-1)$ clock periods. Running at 50 MHz, such a counter repeats after more than five thousand years (5,849 years to be more precise), which is long enough to be irrelevant for most practical purposes.
- Conceptually, a 63-bit LFSR counter consists of a 63-bit shift register, with an XNOR feedback from the last stage and the next-to-last stage.

Table 3: Taps for Maximum-Length LFSR Counters

n	XNOR from	n	XNOR from
3	3,2	45	45,44,42,41
4	4,3	46	46,45,26,25
5	5,3	47	47,42
6	6,5	48	48,47,21,20
7	7,6	49	49,40
8	8,6,5,4	50	50,49,24,23
9	9,5	51	51,50,36,35
10	10,7	52	52,49

Alfke, P.. "Efficient Shift Registers, LFSR Counters, and Long Pseudo Random Sequence Generators." (1995). Online: https://www.xilinx.com/support/documentation/application_notes/xapp052.pdf

